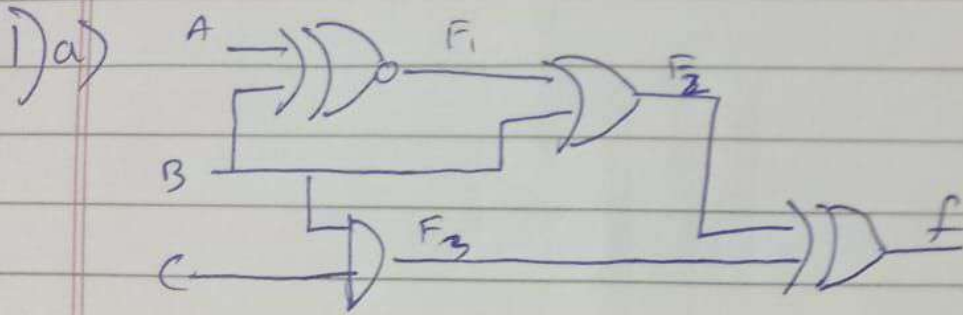


DAY-2 Assignment




$$F_1 = \bar{A}\bar{B} + AB$$

$$\begin{aligned} F_2 &= \bar{A}\bar{B} + AB + B \\ &= \bar{A}\bar{B} + B \Rightarrow \bar{A} + B \end{aligned}$$

$$F_3 = BC$$

$$\begin{aligned} f &= (\underbrace{\bar{A} + B}_X) \oplus \underbrace{BC}_Y \\ &= \bar{X}Y + \bar{Y}X \end{aligned}$$

$$\begin{aligned} \Rightarrow & (\bar{A} + B)(BC) + \overline{(\bar{A} + B)}(BC) \\ & (A\bar{B})(BC) + \bar{A}\bar{B} + \bar{A}C + BC \end{aligned}$$

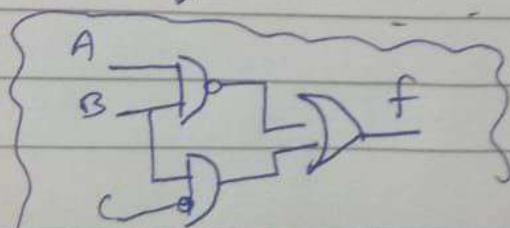Resultant $\downarrow$ 


$$f = \bar{A}B + B\bar{C}$$

($\therefore$ consensus theorem)

$$F_3 = C$$

$$f = B + C$$

Resultant $\rightarrow$

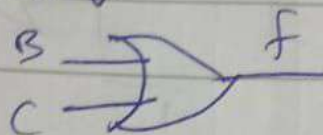

2)

$$a) \bar{A}\bar{C}\bar{D}E + \bar{A}\bar{B}\bar{D} + ABCE + ABD$$

$$\cancel{\bar{A}\bar{D}(C\bar{E} + \bar{B})} + \cancel{AB(C\bar{E} + D)}$$

$$\Rightarrow \underline{\bar{A}\bar{D}(C\bar{E} + \bar{B}) + AB(C\bar{E} + D)}$$

$$b) \bar{A}\bar{B}\bar{C} + ABD + \bar{A}C + \bar{A}C\bar{D} + A\bar{C}D + A\bar{B}\bar{C}$$

$$\Rightarrow \bar{B}\bar{C}(A + \bar{A}) + \bar{A}C(1 + \bar{D}) + AD(B + \bar{C})$$

$$\Rightarrow \bar{B}\bar{C} + \bar{A}C + ADB + \cancel{A\bar{C}D}$$

$$\Rightarrow \underline{\bar{B}\bar{C} + \bar{A}C + ABD}$$

$$c) \bar{A}\bar{C} + BC + A\bar{B} + \bar{A}B\bar{C} + \cancel{A\bar{C}\bar{D}} + \cancel{\bar{B}\bar{C}D}$$

$$\Rightarrow \bar{A}\bar{C}(1 + B) + BC + A\bar{B}$$

$$\Rightarrow \underline{\bar{A}\bar{C} + BC + A\bar{B}}$$

$$d) \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4 + x_2$$

$$\Rightarrow x_2 (1 + x_1 \bar{x}_3 x_4) + \bar{x}_1 \bar{x}_2 x_4 + x_3 x_4 + \bar{x}_1 \bar{x}_3 \bar{x}_4$$

$$\Rightarrow x_2 + \bar{x}_1 x_4 + x_3 x_4 + \bar{x}_1 \bar{x}_3 \bar{x}_4$$

$$\Rightarrow x_1 + x_2 + \bar{x}_1 (x_4 + \bar{x}_3 \bar{x}_4) = x_1 (\bar{x}_3 + x_4) + x_2 + x_3 x_4$$

$$\therefore \bar{x}_1 \bar{x}_3 + x_3 x_4 + x_2 \quad (\because \bar{x}_1 x_4 \text{ neglect})$$

$$3) \text{ Eqn: } Z = (\overline{A \bar{B} \bar{C}}) \oplus (\overline{A \bar{B} C}) (\overline{A B \bar{C}}) (\overline{A B C})$$


$$\therefore \overline{A \bar{B} \bar{C}} + \overline{A \bar{B} C} + \overline{A B \bar{C}} + \overline{A B C}$$

$$\Rightarrow \overline{A \bar{B} \bar{C}} + \overline{A \bar{B} C} + \overline{A B \bar{C}} + \overline{A B C}$$

$$A \oplus B \oplus C$$

\(\therefore\) we use 3 input XOR gate.



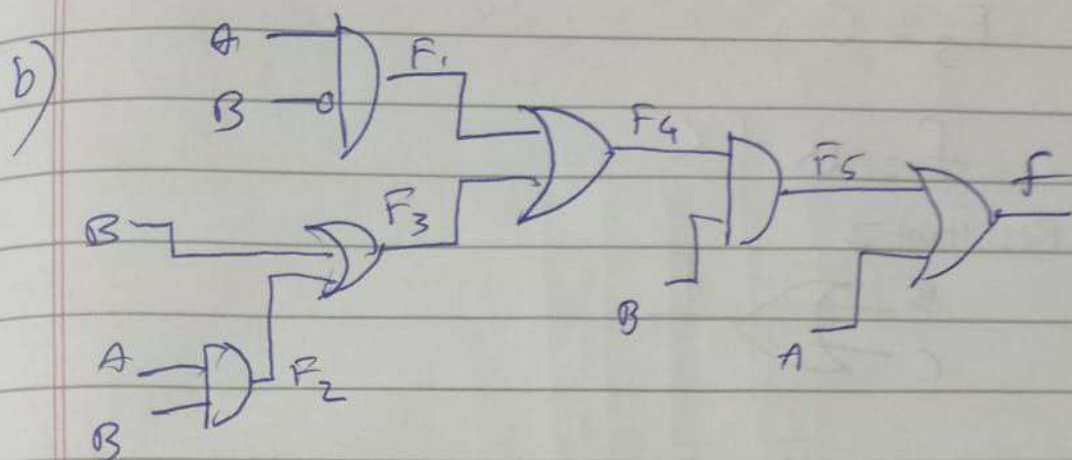



$$F_1 = A\bar{B} \quad F_2 = AB \quad F_3 = B$$

$$F_4 = A + B$$

$$F_5 = AB + B = B$$

$$F_6 = A + B$$


Resultant $\downarrow$

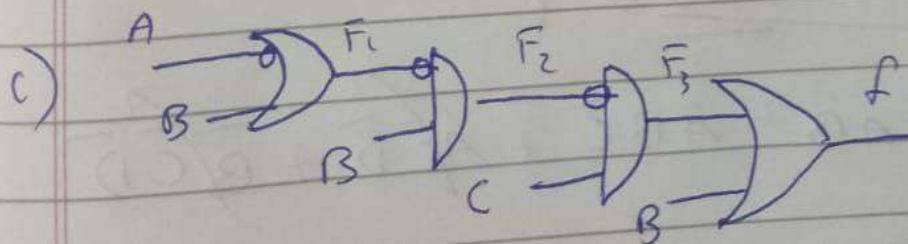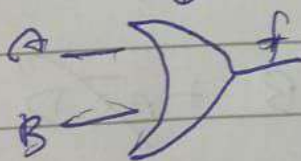

$$F_1 = \bar{A} + B \quad F_2 = (\bar{A} + B) \cdot B$$

$$\Rightarrow 0 \quad \because B \cdot \bar{B} = 0$$

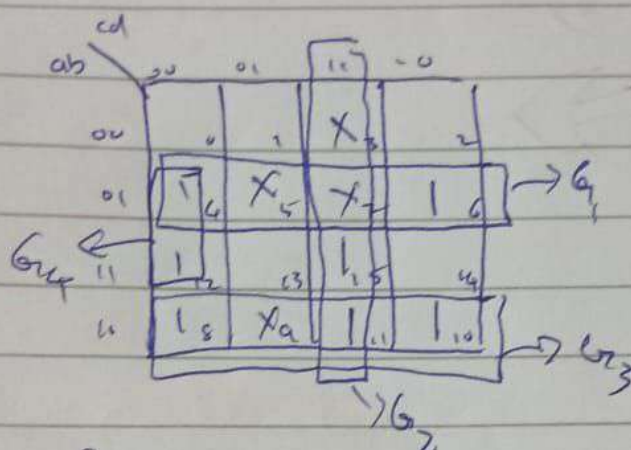
$$4a) f(a, b, c, d) = \Sigma(4, 6, 8, 10, 11, 12, 15) + d(3, 5, 7, 9)$$



$$f = G_1 + G_2 + G_3 + G_4$$

$$= \bar{a}b + cd + a\bar{b} + \bar{a}\bar{c}\bar{d}$$
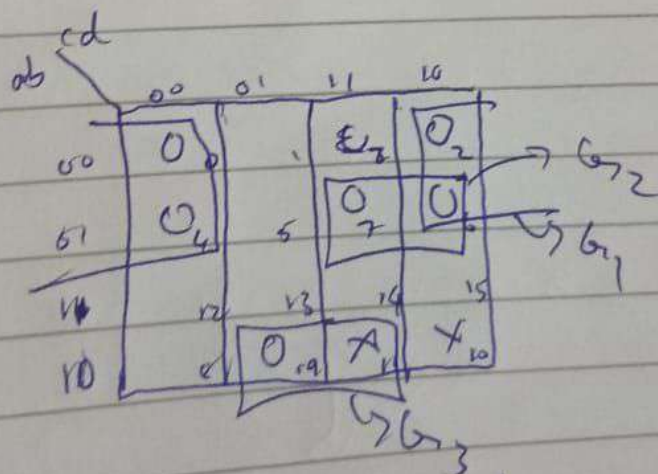
$$b) f(a, b, c, d) = \prod(0, 2, 4, 6, 7, 9) \cdot d(10, 11)$$



$$f = G_1 + G_2 + G_3$$

$$f = (a+d)(a+b+c)(a+b+d)$$