

DAY 3 - Assignment.

1)

a) $F(A, B, C) = \bar{A}C + B\bar{C}$

convert into canonical:


$$\bar{A}C(B + \bar{B}) + B\bar{C}(A + \bar{A})$$

$$\bar{A}BC + \bar{A}\bar{B}C + AB\bar{C} + \bar{A}B\bar{C}$$

T.T:


→ ~~Sum~~

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

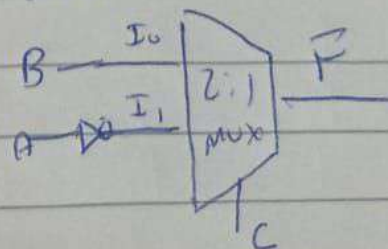i) looking at eqⁿ: $\bar{A}C + B\bar{C}$ if $C=0$: $F=B$ $C=1$: $F=\bar{A}$ 

ii)

A	B	F
0	0	0
0	1	1
1	0	0
1	1	1

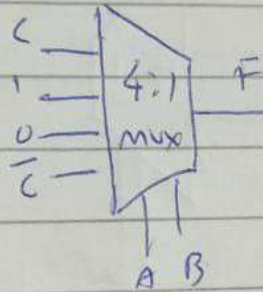


$$b) \bar{P}\bar{R} + Q\bar{R} + \bar{P}Q = F(P, Q, R)$$

$$F(P, Q, R) = \bar{P}\bar{R}Q + \bar{P}\bar{R}\bar{Q} + \bar{P}RQ + P\bar{R}Q + \bar{P}R\bar{Q} + \bar{P}\bar{R}Q$$


$$\Rightarrow \bar{R}(\bar{P}Q + \bar{P}\bar{Q} + P\bar{Q}) + R(\bar{P}Q)$$

$$\bar{R}(\bar{P} + Q) + R(\bar{P}Q)$$


taking R as select lines:

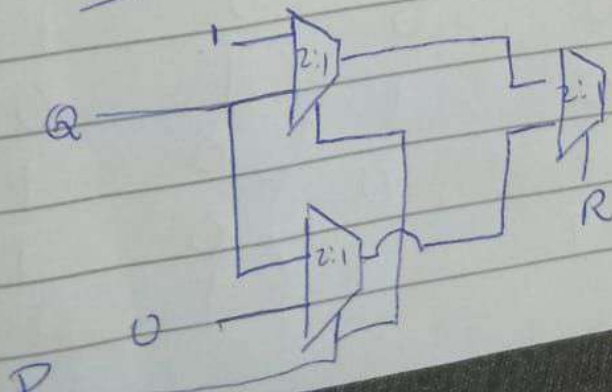


For Sum: using 2 MUX
 MUX 1: for $A \oplus B$

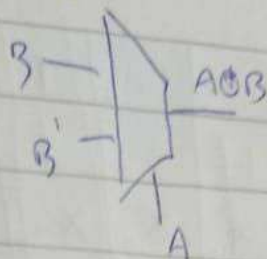


MUX 2: $A \oplus B \oplus C_{in}$

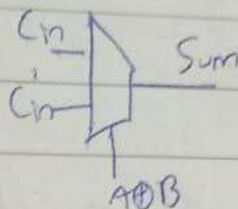

Finally:

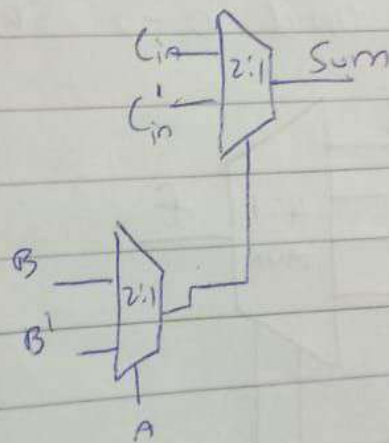


For carry:

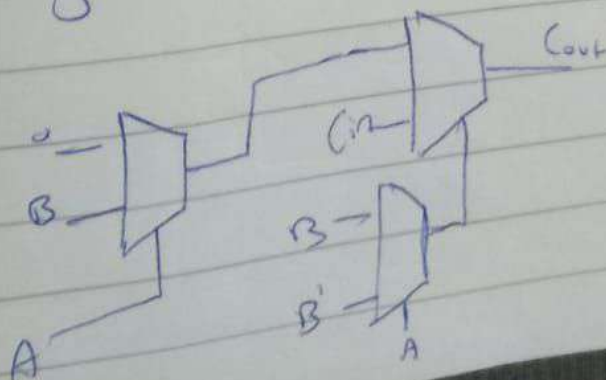

i) P Q F

0	0	$\bar{R}$
0	1	1
1	0	0
1	1	R

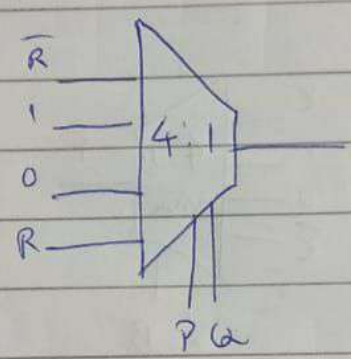

2) FA using 2:1 MUX


S, C (A, B, C_{in})

$$S = A \oplus B \oplus C_{in}$$

A	B	C_{in}	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

3) $f(a, b, c, d) = \sum (2, 4, 5, 6, 10) + D(12, 13, 14, 15)$

Solⁿ

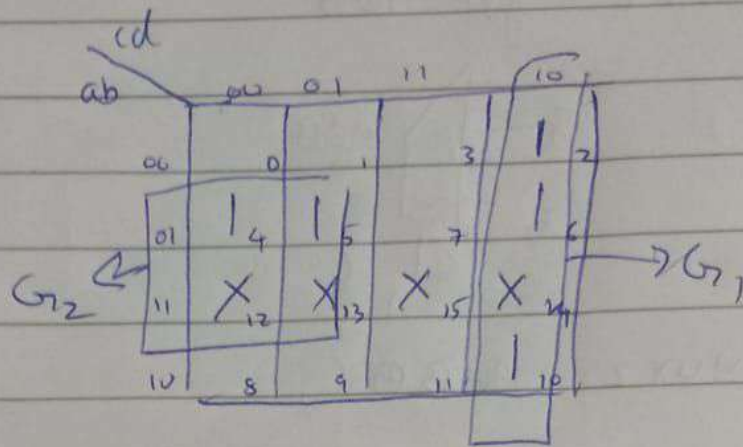

using k-maps:

$$f = b\bar{c} + cd$$

$$\Rightarrow \cancel{abc\bar{c}} + \cancel{ab\bar{c}} + \cancel{ab\bar{c}} + \cancel{ab\bar{c}}$$

let a and $b \rightarrow$ select lines

